

# Project : Digital Pulse Oximeter.

## Principle:

1). Beer's Law:  $I = I_0 \cdot 10^{-\epsilon CL}$

$I_0$ : light intensity entering sample.

$I$ : ~ leaving sample.

$\epsilon$ : extinction coefficient

$C$ : sample concentration

$L$ : sample length (depth)

2) Absorbance of Hemoglobin (Hb) and Oxygenated Hemoglobin ( $HbO_2$ ) at various wavelength.


Absorbance:

$$A = \epsilon CL.$$

\* assume  $C$  and  $L$  constant.


$C = 1 \text{ mmol}$

$L = 1 \text{ cm}$

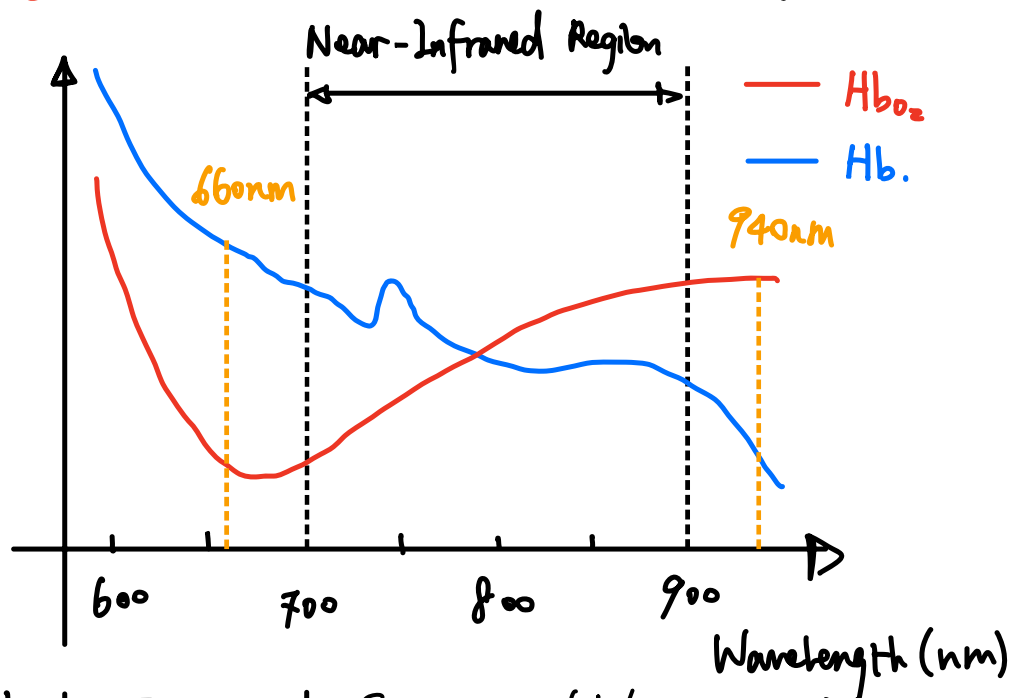

wavelength	$\epsilon_{Hb}$	$\epsilon_{HbO_2}$	( $L/(\text{mmol} \cdot \text{cm})$ )
660	0.81	0.08	
940	0.18	0.29	

# Modeling of Finger.

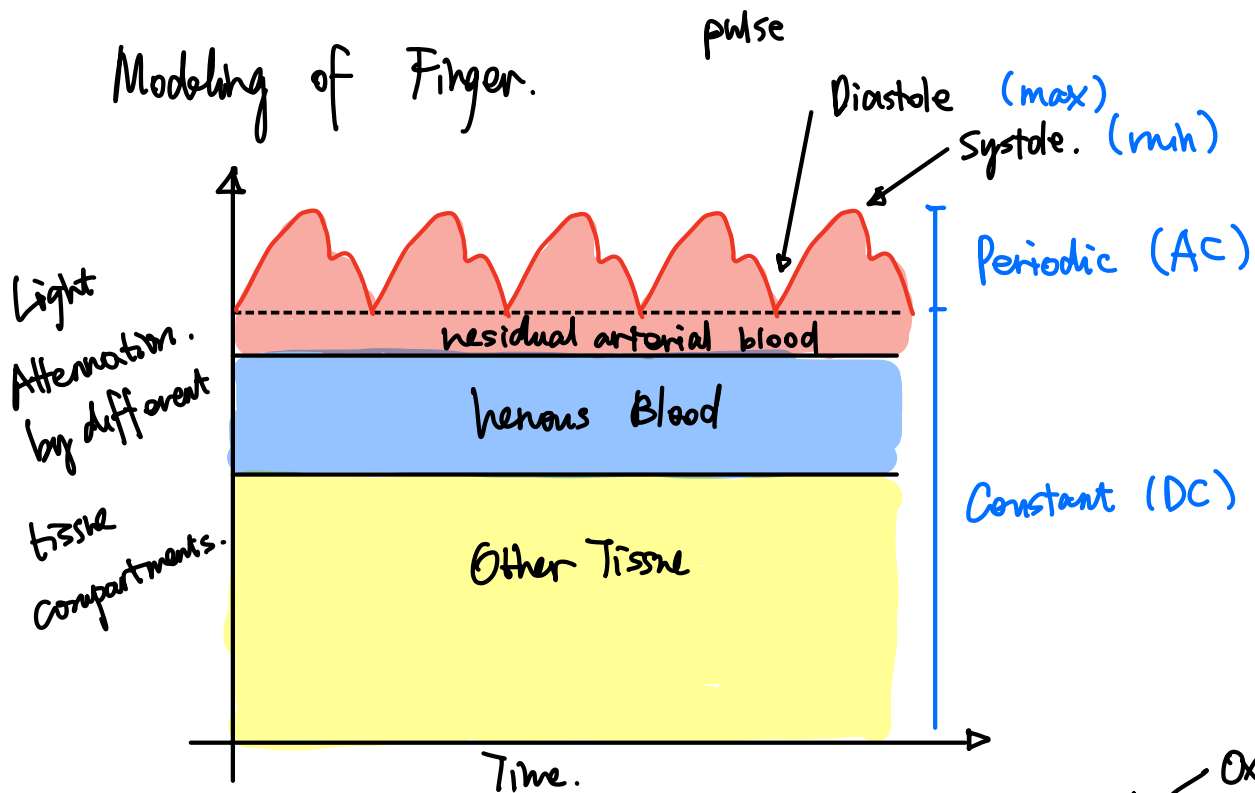

at systole:

$$I_{min} = I_0 10^{-\epsilon_{DC} C_{DC} L_{DC} - (\epsilon_{Hb} C_{Hb} + \epsilon_{HbO_2} C_{HbO_2}) L_{max}}$$

at diastole:

$$I_{max} = I_0 10^{-\epsilon_{DC} C_{DC} L_{DC} - (\epsilon_{Hb} C_{Hb} + \epsilon_{HbO_2} C_{HbO_2}) L_{min}}$$

ratio:

$$\frac{I_{min}}{I_{max}} = \frac{I_0 10^{-\epsilon_{DC} C_{DC} L_{DC} - (\epsilon_{Hb} C_{Hb} + \epsilon_{HbO_2} C_{HbO_2}) L_{max}}}{I_0 10^{-\epsilon_{DC} C_{DC} L_{DC} - (\epsilon_{Hb} C_{Hb} + \epsilon_{HbO_2} C_{HbO_2}) L_{min}}}$$

$$= 10^{-\cancel{\epsilon_{DC} C_{DC} L_{DC}} - (\epsilon_{Hb} C_{Hb} + \epsilon_{HbO_2} C_{HbO_2}) (L_{max} - L_{min}) + \cancel{\epsilon_{DC} C_{DC} L_{DC}}}$$

$$= 10^{-(\epsilon_{Hb} C_{Hb} + \epsilon_{HbO_2} C_{HbO_2}) \Delta L}$$

$$\Rightarrow \log \frac{I_{min}}{I_{max}} = -(\epsilon_{Hb} C_{Hb} + \epsilon_{HbO_2} C_{HbO_2}) \Delta L$$

$$A = (\epsilon_{Hb} C_{Hb} + \epsilon_{HbO_2} C_{HbO_2}) \Delta L = \log \frac{I_{max}}{I_{min}}$$

$$\Rightarrow C_{Hb} = \frac{A}{\Delta L} - \frac{\epsilon_{HbO_2} C_{HbO_2}}{\epsilon_{Hb}}, \quad C_{HbO_2} = \frac{A}{\Delta L} - \frac{\epsilon_{Hb} C_{Hb}}{\epsilon_{HbO_2}}$$

at  $\lambda_1$  and  $\lambda_2$  (660nm and 940nm to maximize diff's)

$$A_{\lambda_1} = (\epsilon_{Hb, \lambda_1} C_{Hb} + \epsilon_{HbO_2, \lambda_1} C_{HbO_2}) \Delta L$$

$$A_{\lambda_2} = (\epsilon_{Hb, \lambda_2} C_{Hb} + \epsilon_{HbO_2, \lambda_2} C_{HbO_2}) \Delta L$$

$$\frac{A_{\lambda_1}}{A_{\lambda_2}} = \frac{\epsilon_{Hb, \lambda_1} C_{Hb} + \epsilon_{HbO_2, \lambda_1} C_{HbO_2}}{\epsilon_{Hb, \lambda_2} C_{Hb} + \epsilon_{HbO_2, \lambda_2} C_{HbO_2}}$$

$$(\epsilon_{Hb, \lambda_2} C_{Hb} + \epsilon_{HbO_2, \lambda_2} C_{HbO_2}) A_{\lambda_1} = (\epsilon_{Hb, \lambda_1} C_{Hb} + \epsilon_{HbO_2, \lambda_1} C_{HbO_2}) A_{\lambda_2}$$

$$C_{Hb} (\epsilon_{Hb, \lambda_2} A_{\lambda_1} - \epsilon_{Hb, \lambda_1} A_{\lambda_2}) = C_{HbO_2} (\epsilon_{HbO_2, \lambda_1} A_{\lambda_2} - \epsilon_{HbO_2, \lambda_2} A_{\lambda_1})$$


$$\Rightarrow C_{Hb} = C_{HbO_2} \frac{(\epsilon_{HbO_2, \lambda_1} A_{\lambda_2} - \epsilon_{HbO_2, \lambda_2} A_{\lambda_1})}{(\epsilon_{Hb, \lambda_2} A_{\lambda_1} - \epsilon_{Hb, \lambda_1} A_{\lambda_2})}$$

$$S_{pO_2} = \frac{C_{HbO_2}}{C_{HbO_2} + C_{Hb}} = \frac{\cancel{C_{HbO_2}}}{\cancel{C_{HbO_2}} \left( 1 + \frac{(\epsilon_{HbO_2, \lambda_1} A_{\lambda_2} - \epsilon_{HbO_2, \lambda_2} A_{\lambda_1})}{(\epsilon_{Hb, \lambda_2} A_{\lambda_1} - \epsilon_{Hb, \lambda_1} A_{\lambda_2})} \right)}$$

$$= \frac{(\epsilon_{Hb, \lambda_2} A_{\lambda_1} - \epsilon_{Hb, \lambda_1} A_{\lambda_2})}{(\epsilon_{Hb, \lambda_2} A_{\lambda_1} - \epsilon_{Hb, \lambda_1} A_{\lambda_2}) + (\epsilon_{HbO_2, \lambda_1} A_{\lambda_2} - \epsilon_{HbO_2, \lambda_2} A_{\lambda_1})}$$


or = \_\_\_\_\_

# Theoretical Schematic

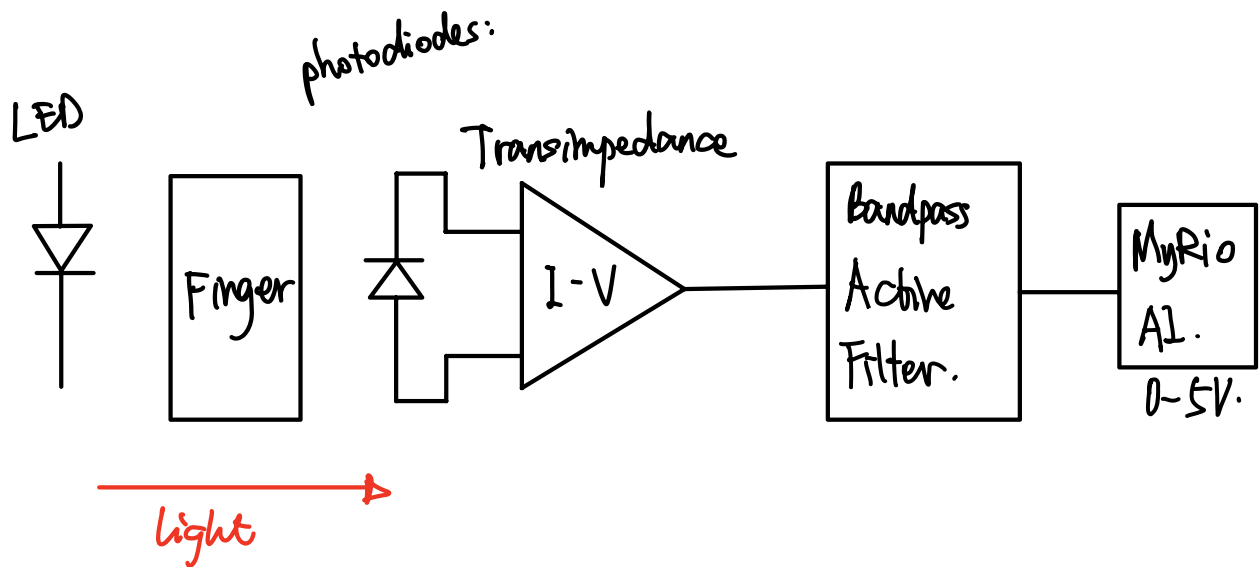

• Power.


• Transimpedance Amplifier.

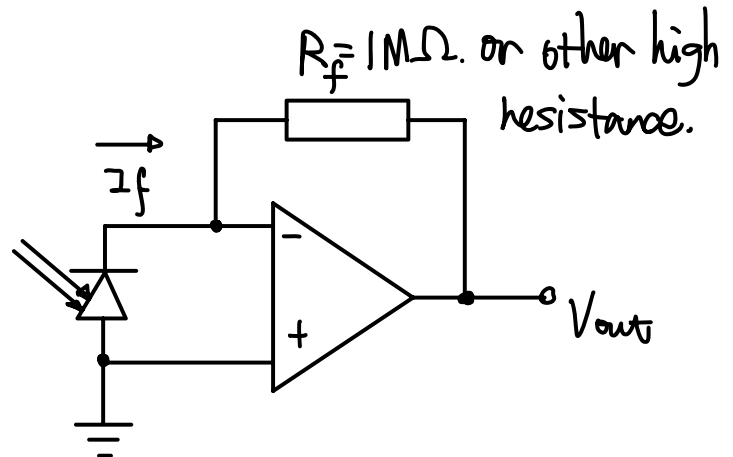

- Measure idle. voltage / finger-inserted voltage.  
compare to myRio AI. port.

$$V_{out} = -I_f R_f.$$


• Bandpass Active Filter

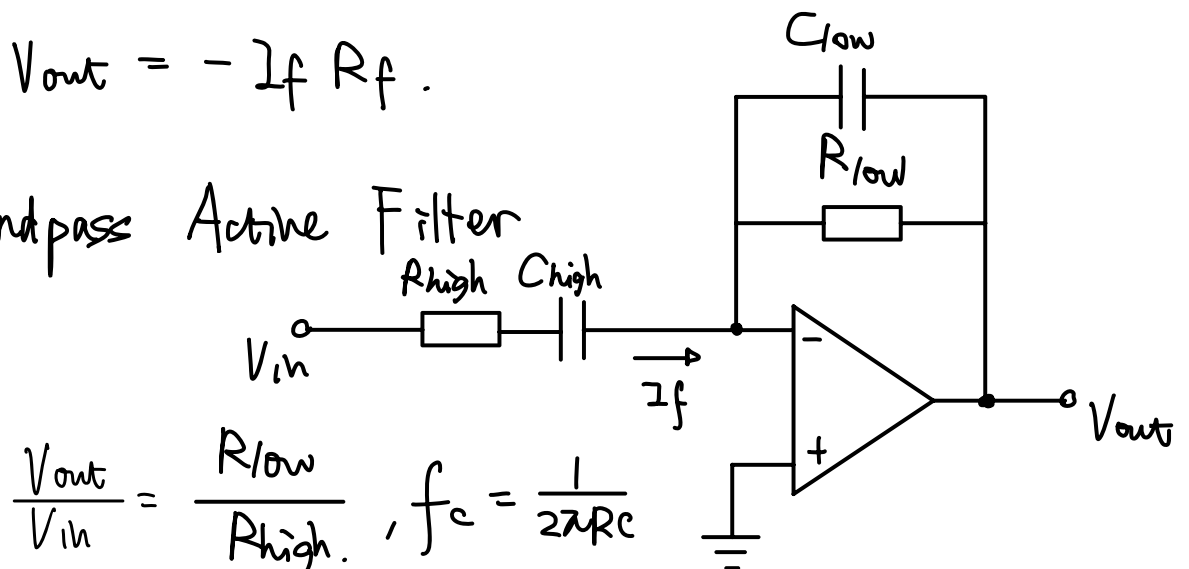

$$\frac{V_{out}}{V_{in}} = \frac{R_{low}}{R_{high}}, f_c = \frac{1}{2\pi RC}$$




✗ color code:  $V_{CC}$  GND Signal (Red) Signal (GR)

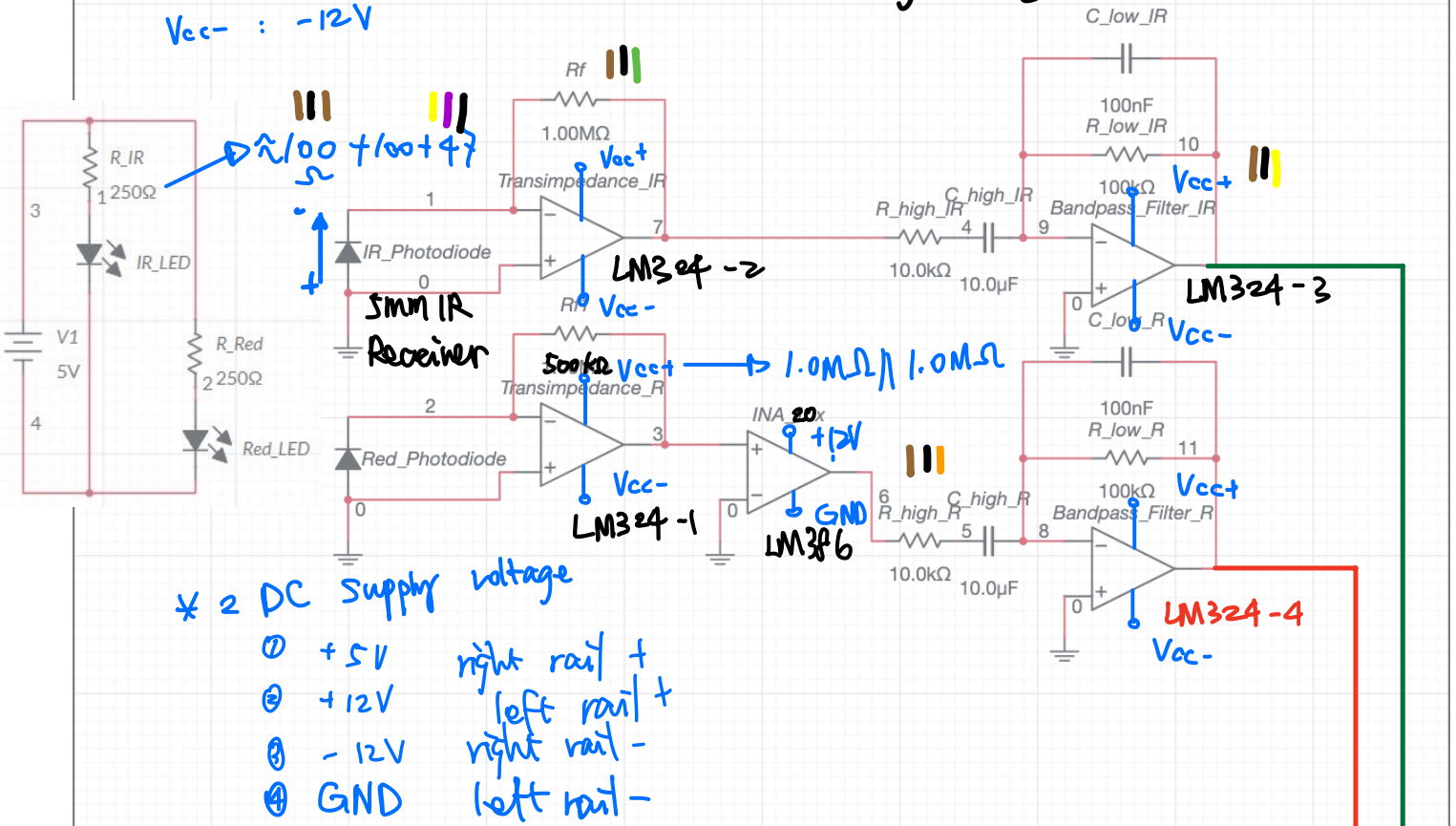\* common mode voltage  $\frac{1}{2} \text{sum}(I_{N+}, I_{N-})$



\* 2 DC Supply voltage

①	+5V	right rail +
②	+12V	left rail +
③	-12V	right rail -
④	GND	left rail -

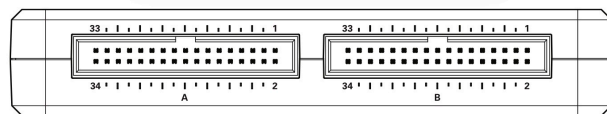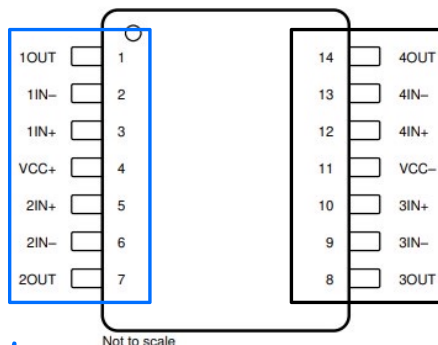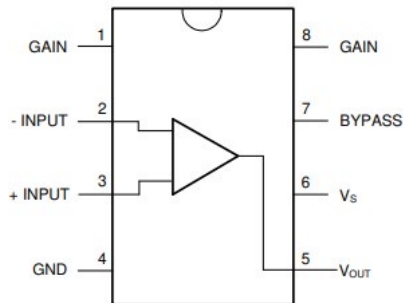

DIO15 / I2C.SDA	33	31	DIO9 / PWM1	+3.3 V
DIO14 / I2C.SCL	32	29	DIO8 / PWM0	DIO10 / PWM2
DGND	30	27	DIO7 / SPI.MOSI	DIO9 / PWM1
DGND	28	25	DIO6 / SPI.MISO	DIO8 / PWM0
DIO13	26	23	DIO5 / SPI.CLK	DIO7 / SPI.MOSI
DGND	24	21	DIO4	DIO6 / SPI.MISO
DIO12 / ENC.B	22	19	DIO3	DIO5 / SPI.CLK
DGND	20	17	DIO2	DIO4
DIO11 / ENC.A	18	15	DIO1	DIO3
DGND	16	13	DIO0	DIO2
UART.TX	14	11	A13	DIO1
DGND	12	9	A12	DIO0
UART.RX	10	7	A11	A13
DGND	8	5	A10	A12
AGND	6	3	+5V	A11
A01	4	1		A10
A00	2			+5V

Trans-impedance Not to scale Active filter.

Resistor choice: (based on LM324; LM386 has preset gains)


LM324:

- bias current ( $i_b$ )

$$\leq \pm 35 \text{ nA}$$

- input impedance ( $R_{in}$ )

$$= 1 \text{ G}\Omega$$

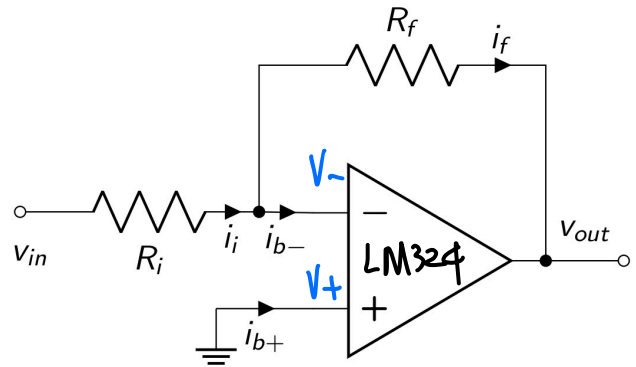

To avoid signal clipping at A10, let ideal output

$$V_{out,i} = 5V \cdot 90\% = -4.5V$$

and the error tolerance 1%

$$\text{in worst case } V_{out} = (1 - 1\%) \times V_{out,i} = -4.4550V$$

assume ideal non-inverting input & virtual short.

$$V_- = V_+ = 0V$$

$$i_f = \frac{V_- - V_{out}}{R_f} = \frac{4.4550V}{R_f}$$

$$V_{in} = -V_{out,i} \cdot \frac{R_i}{R_f} = 4.5V \cdot \frac{R_i}{R_f}$$

$$i_i = \frac{V_{in} - V_-}{R_i} = \frac{V_{in}}{R_i} = \frac{4.5V}{R_f}$$

According to KCL (at - input node):  $i_i = i_{b-} + i_f$

$$i_{b-} = i_i - i_f \quad \text{and} \quad i_{b-} = 35 \text{ nA} = \frac{4.5V - 4.4550V}{R_f}$$

$$\text{so } R_{f, \text{upper}} = \frac{(4.5 - 4.4550)V}{35 \times 10^{-9} A} = 1.3 \times 10^6 \Omega = 1.3 M\Omega$$

• however, the input impedance  $R_{in} = 1 G\Omega$

we want  $R_f \ll R_{in}$


\* the desired upper bound of  $R_f$  is around  $130 k\Omega$

• output impedance ( $R_{out}$ )

$$= 300 \Omega$$

• output current ( $I_{out}$ )

$$\leq -60 mA$$

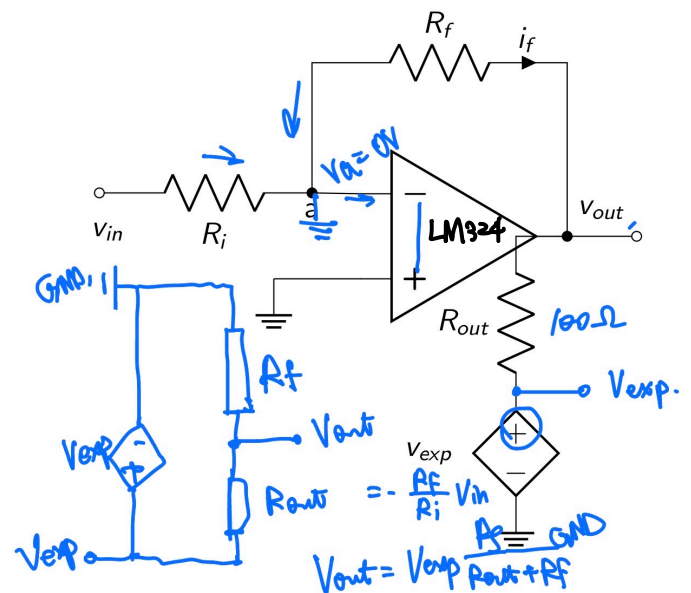

\* assume input side fully ideal,  $V_a = 0V$

the output impedance  $R_{out}$  forms a voltage divider with  $R_f$   
if we would like **99% preserved**  $\frac{V_{out}}{V_{exp}}$

$$V_{out} = V_{exp} \cdot \frac{R_f}{R_f + R_{out}} \Rightarrow \frac{R_{f, \text{lower}}}{R_{f, \text{lower}} + 300 \Omega} = 0.99$$


$$\Rightarrow R_{f, \text{lower}} = 29.7 k\Omega$$

Thus for LM324:  $30 k\Omega \leq R_f \leq 130 k\Omega$

# Labview Program Design:

① Super Loop vs. Producer consumer loop.

Super Loop:

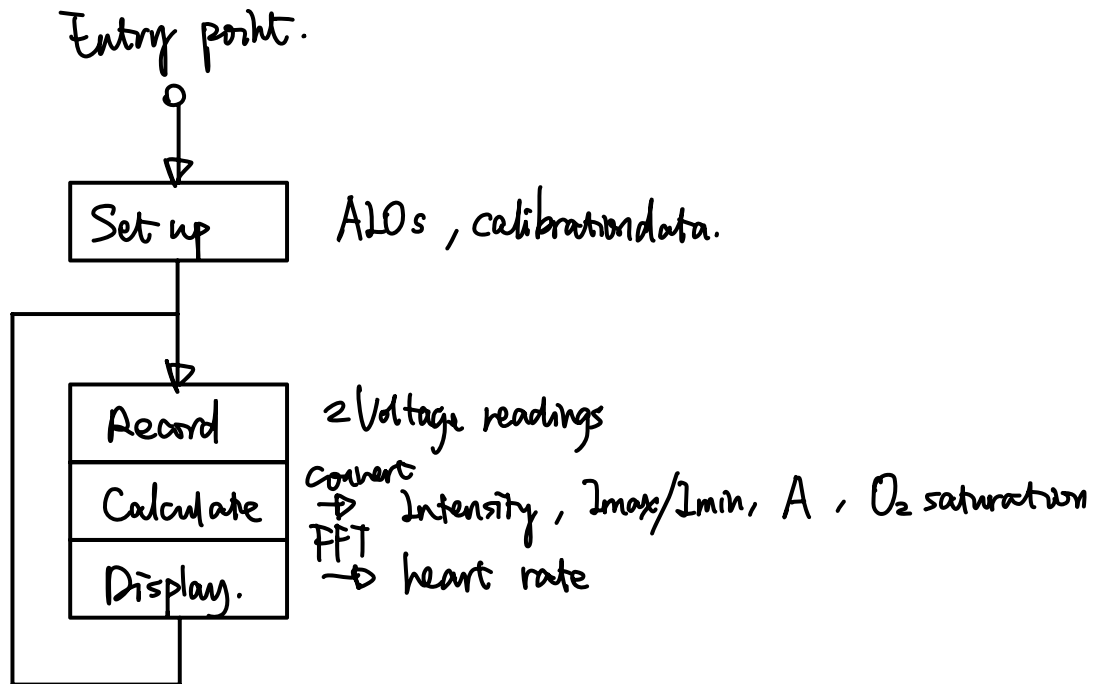



② Sub  $V_L$  :